

QUESTIONSHEET 1

(a) $3 \text{ A} / 2$	1
$= 1.5 \text{ A}$	1
(b) 6 V	1
(c) resistance $= V / I$	1
$= 6 / 1.5$	1
$= 4 \Omega$	1
	TOTAL / 6


QUESTIONSHEET 2

(a) $5 \Omega + 10 \Omega$	1
$= 15 \Omega$	1
(b) $I = V / R$	1
$= 3 / 15$	1
$= 0.2 \text{ A}$	1

Units are essential in calculations. Sometimes examination questions give a blank space for the answer followed by the unit. Sometimes no unit is given and you are expected to supply it. It is a common mistake to leave the units out altogether – don't get into this bad habit.

TOTAL / 5

QUESTIONSHEET 3

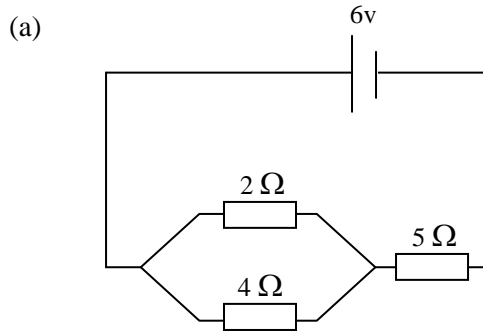

symbols correct

2 Ω and 4 Ω resistors in parallel

5 Ω resistor in series

1
1
1

(b) resistance of parallel resistors given by

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{2} + \frac{1}{4}$$

$$R_t = \frac{4}{3} \Omega$$

$$\text{so total resistance} = \frac{4}{3} \Omega + 5 = 6\frac{1}{3} \Omega$$

1
1
1
1

(c) $\frac{6}{6\frac{1}{3}}$
= 0.95 A

1
1

For parallel resistors, it is sometimes easier to use the expression Product / Sum for the total resistance.
i.e. here we get $2 \times 4 / (2 + 4) = 8 / 6 = 4/3 \Omega$

TOTAL / 9

QUESTIONSHEET 4

- (a) (i) Power of lamp is 6 W 1
when used on 12 V 1
- (ii) $6 \text{ W} = 6 \text{ J/s}$ 1
 $5 \text{ minutes} = 300 \text{ s}$ 1
energy transferred = 300×6 1
 $= 1800 \text{ J}$ 1
- (b) (i) $I = P / V = 6 / 12$ 1
 $= 0.5 \text{ A}$ 1
- (ii) $R = V / I = 12 / 0.5$ 1
 $= 24 \Omega$ 1
- (c) No difference 1
24 V shared between 2 lamps / pd across each lamp is 12 V 1

Power is the rate of transferring electrical energy into other forms – in this case, heat and light. A 6 W lamp transfers 6 Joules of electrical energy into heat & light each second, since $1 \text{ W} = 1 \text{ J/s}$.
The formula $P = I \times V$ is one you need to know.

TOTAL / 12**QUESTIONSHEET 5**

- (a) (i) $0.6 \times 10/20$ 1
 $= 0.3 \text{ A}$ 1
- (ii) $0.6 + 0.3$ 1
 $= 0.9 \text{ A}$ 1
- (b) $V = I R$ 1
 0.6×10 or 0.3×20 1
 $= 6 \text{ V}$ 1

Current is inversely proportional to the resistance as long as the pd is constant. So half the current flows through the resistor that is twice as big.

TOTAL / 7

QUESTIONSHEET 6

- (a) $\frac{1}{R} = \frac{1}{10} + \frac{1}{10} = \frac{1}{5}$ 1
 $R = 5 \Omega$ 1
- (b) $10 + 5$ 1
 $= 15 \Omega$ 1
- (c) current through single resistor $= V / R = 6 / 15$ 1
 $= 0.4 \text{ A}$ 1
current through parallel resistors $= 0.2 \text{ A}$ 1

In many questions, the value of the parallel resistors is the same. In this case, the total resistance is half the value of one.

TOTAL / 7

QUESTIONSHEET 7

- (a) (i) $2 + 5 + 10$ 1
 $= 17 \Omega$ 1
- (ii) $1/R = 1/2 + 1/5 + 1/10$ 1
 $= 8 / 10 \Omega$ 1
 $R = 10 / 8 = 1.25 \Omega$ 1
- (b) Current larger in (ii) 1
current inversely proportional to resistance 1
smaller resistance means larger current 1

TOTAL / 8

QUESTIONSHEET 8

- (a) $\frac{1}{R_1} = \frac{1}{6} + \frac{1}{12} = \frac{1}{4} \Rightarrow R_1 = 4\Omega$ 1
- $\frac{1}{R_2} = \frac{1}{3} + \frac{1}{6} = \frac{1}{2} \Rightarrow R_2 = 2$ 1
- Total resistance = $2 + 4 = 6\Omega$ 1
- (b) $I = V / R$ 1
 $= 12 / 6$ 1
 $= 2 \text{ A}$ 1
- (c) $R = 4 + 3$ 1
 $= 7$ 1
 $I = 12 / 7$ or 1.7 A 1
- (d) $R = 3 + 6 = 9 \Omega$ 1
 $I = V / R = 12 / 9$ 1
 $= 1.33 \text{ A}$ 1

TOTAL / 11**QUESTIONSHEET 9**

- (a) C 1
- (b) (i) a complete path 1
for electricity to flow 1
when connected to a voltage supply 1
- (ii) A & D (both) 1


No electricity flows in the last circuit, because the cells are the opposite way round from each other, so they cancel out.

TOTAL / 5

QUESTIONSHEET 10

(a) switch shown in either of the positions indicated

1

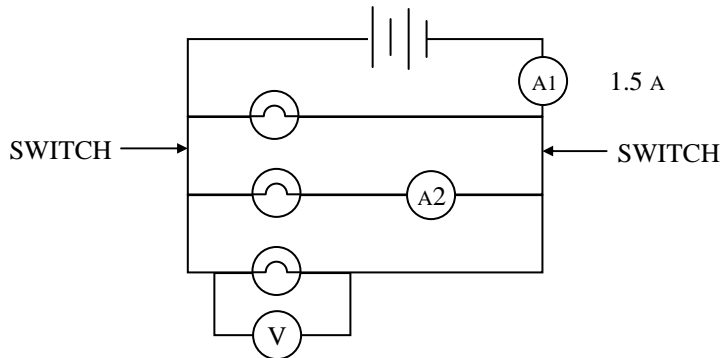

(b) Parallel

1

(c) $1.5 / 3$
 $= 0.5 \text{ A}$

1

1

(d) 12 V

1

TOTAL / 5**QUESTIONSHEET 11**

(a) Resistance in circuit alters current

1

ammeter resistance must be low so it doesn't affect
current flow

1

(b) (i) In parallel across component

1

(ii) voltmeter must have high resistance
little current flows through voltmeter
most current flows through component

1


1

1

For two parallel resistors, $1/R = 1/R_1 + 1/R_2$. So if one resistor (the voltmeter) R_2 has a high resistance, $1/R_2$ is very small and the total resistance is almost the same as without the voltmeter.

TOTAL / 6

QUESTIONSHEET 12

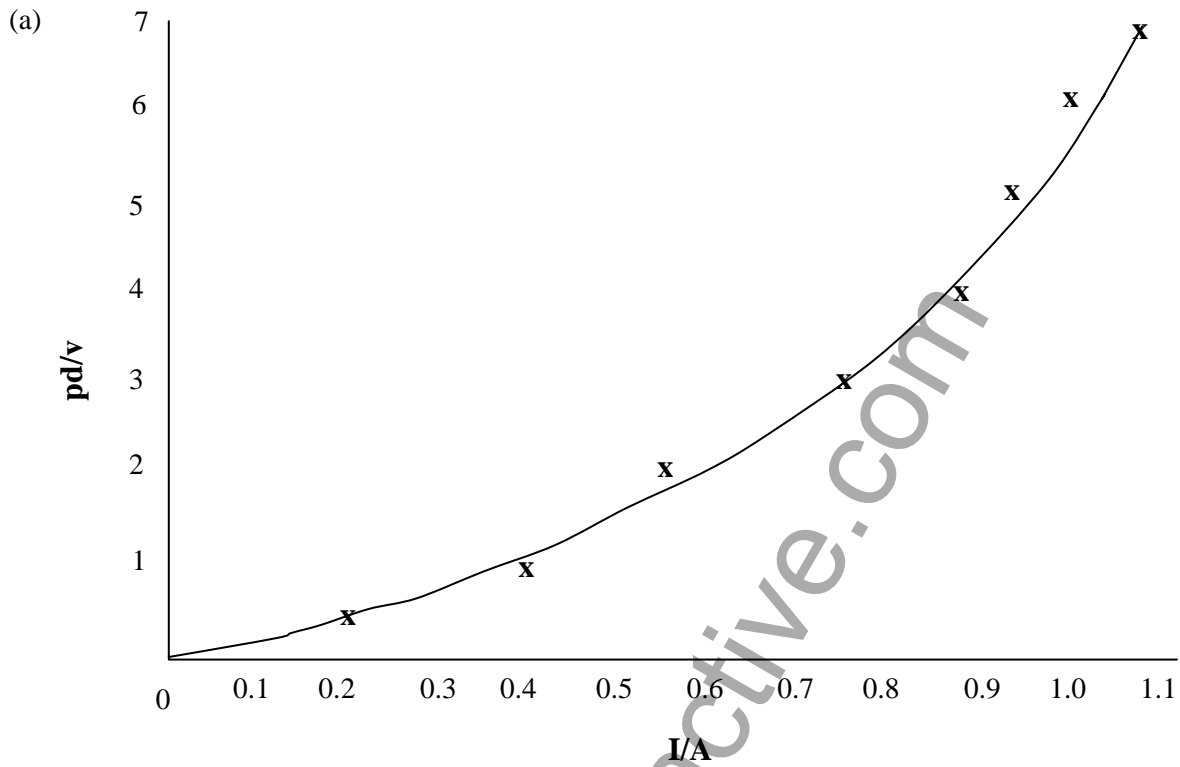

axes labelled + units
correct plotting
smooth curve drawn

1
2
1

(b)(i) no

1

(ii) the graph is not a straight line
or $V / A \neq R$

1
1

(iii) filament lamp


1

TOTAL / 8

QUESTIONSHEET 13

- (a) Voltage is proportional to current
for a metal conductor at constant temperature

1
1

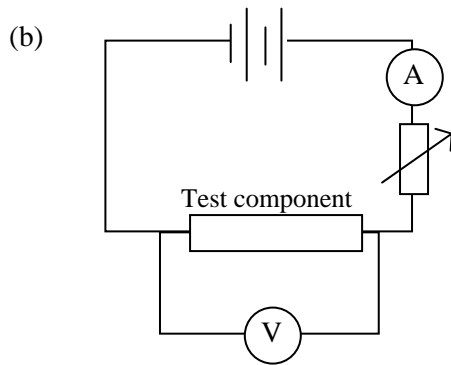

- circuit symbols correct
ammeter in series
voltmeter in parallel
variable resistor in series

1
1
1
1

TOTAL / 6

QUESTIONSHEET 14

- (a) A = metal wire
B = diode
C = lamp filament

1
1
1

(b) A

1

(c) C


1

An ohmic conductor obeys Ohm's law, so a graph of I against V must be a straight line through the origin.
The gradient of graph C decreases so the resistance must be increasing.

TOTAL / 5

QUESTIONSHEET 15

(a) (i)

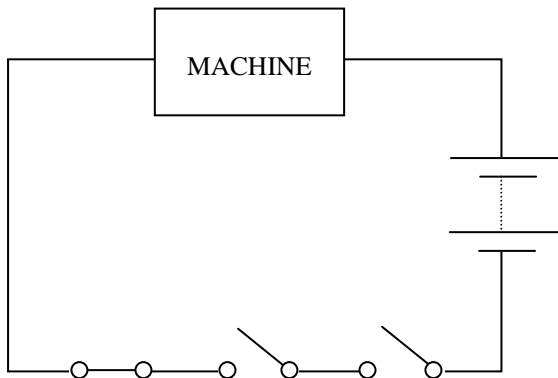

two switches
in series
with machine

1
1
1

(ii) each switch must be able to turn off machine

1


(b) switches not in series
each must be able to switch light on or off
needs two parallel parts of circuit

1
1
1

TOTAL / 7


QUESTIONSHEET 16

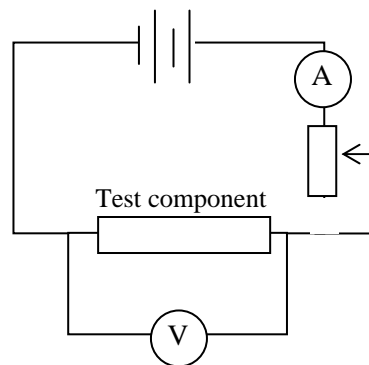- (a) Set up Ohm's law circuit
measure pd across wire and current through it
measure length of wire
change length of wire and repeat experiment



1
1
1
1

(b)(i)

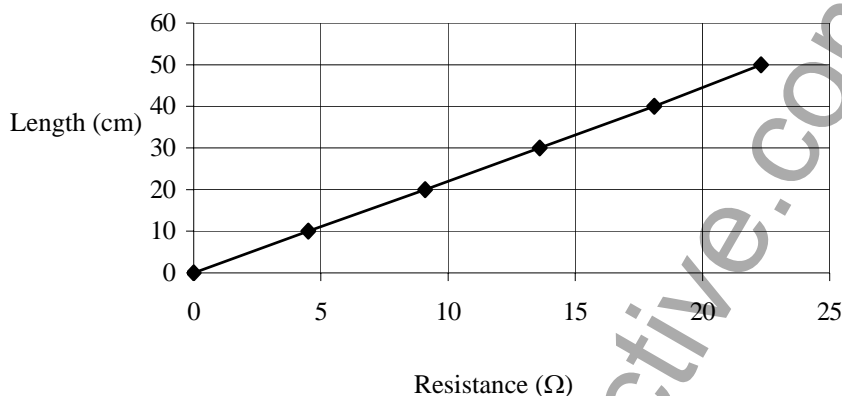

- (ii) as length increases
resistance increases
directly proportional

- (iii) as length varies, resistance varies
current varies
and light dims or brightens

1
1
1
1
1

The first two or three marks of this question could be obtained by drawing a labelled diagram.

TOTAL / 12

QUESTIONSHEET 17

- (a) A = battery
B = lamp/light bulb
C = switch
D = variable resistor

1
1
1
1

- (b) varies current in a circuit / acts as dimmer switch

1

You must be able to recognise circuit components. Look at the syllabus or ask your teacher which ones you must know. Note that a battery is made up of two or more cells joined in series

TOTAL / 5

QUESTIONSHEET 18

(a) (i) 1.5 V	1
(ii) 0 V	1
(iii) 3.0 V	1
(iv) 1.5 V	1
(v) 1.5 V	1
 (b) car bulb needs 12 v	 1
 (c) increases	 1
TOTAL / 7	

QUESTIONSHEET 19

(a) silver too expensive	1
(b) copper is too heavy	1
(c) rubber and PVC	2
(d) water will conduct electricity would get shock with wet hands	1 1
TOTAL / 7	

QUESTIONSHEET 20

(a) One connected after another in line	2
(b) 240 / 20 = 12 V	1 1
(c) bulb from 40-bulb set uses 6 v higher voltage would cause it to blow	1 1
(d) (i) fuse would blow repeatedly	1
(ii) fault would not blow fuse could be dangerous to operator	1 1
TOTAL / 9	
